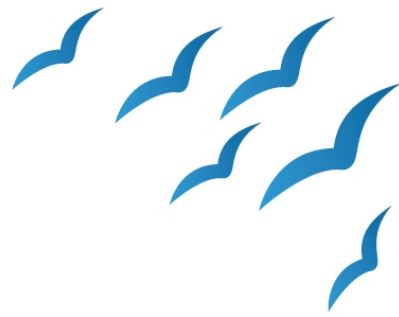


The Alachua County “QUINTPlexor”

Gordon Gibby KX4Z






Driven by ARRL FIELD DAY....

We started with simple BandPass Filters

- Goal was simply to be able to operate multiple stations with Field Day antennas not that far apart and still be able to operate.
- Our filter experience was near zero.


ARRL Butterworth Filters

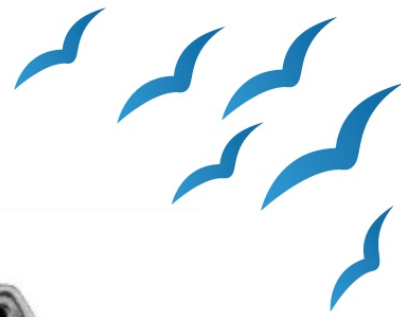

Band-Pass Filters for HF Transceivers

Do your multiple-transmitter Field Day or contest efforts suffer from intrastation interference? These handy and inexpensive filters can help!

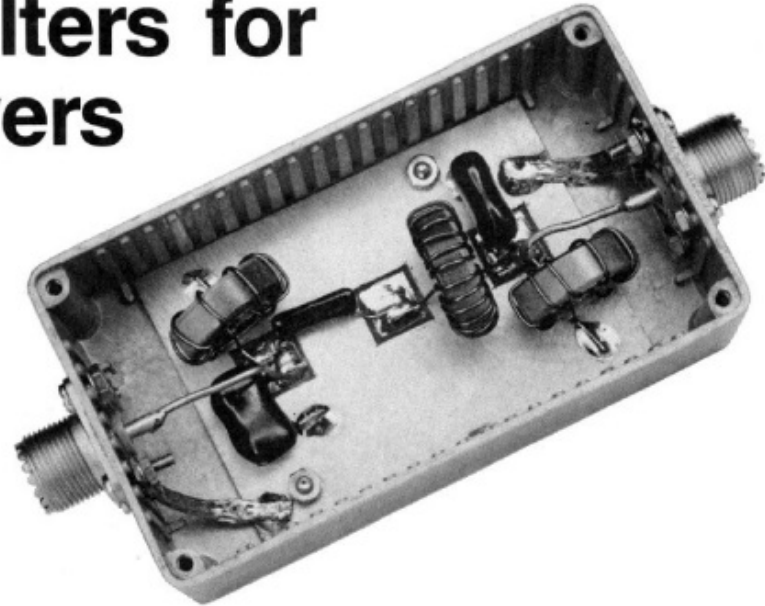By Lew Gordon, K4VX
PO Box 105
Hannibal, MO 63401



One of the more aggravating aspects of competitive Amateur Radio operation comes when you're all set up for Field Day or a DX contest in a multiple-transmitter category and you discover an intrastation interference problem. All that planning and anticipation appears to be headed down the drain! Frustrations and tempers immediately mount: Someone yells "Eighty meters is wiping me out!" or someone else screams "Every time you

band phase-noise interference is not usually a major problem unless stations are operating in close physical proximity, as is the case in Field Day or multitransmitter contest operations.

In seeking a solution to the intrastation interference problem that I could apply in my multitransmitter DX-contest station, I first entertained the idea of constructing large, high-power-handling band-pass filters for each transmitter. These filters would not only reduce the transmitted noise

tion, this scheme would provide filtering during receiving, helping to reduce front-end overload problems. The best part is that even if you use all new components, the cost of these filters should not exceed \$10 each. All that's necessary for tune up is a dip meter and a general coverage receiver. These filters were first described in an article I wrote for the *National Contest Journal*.²

Filter Design and Construction

Perhaps driven by cost / availability, author recommends relatively SMALL toroids and allows For 500V capacitors.... These are a BEAR to tune....complex interactions




Tolerable Bandpass Filter Results

- Insertion losses 0.5-1 dB
- “Next-Band” separation nothing to write home about – 20 dB? Between 20meters and 15 meters not so good.....
- Tremendous help in Field Day when combined with
 - Attenuation added in receiver
 - IP+ turned on, ICOM 7300



Our EOC Problem:

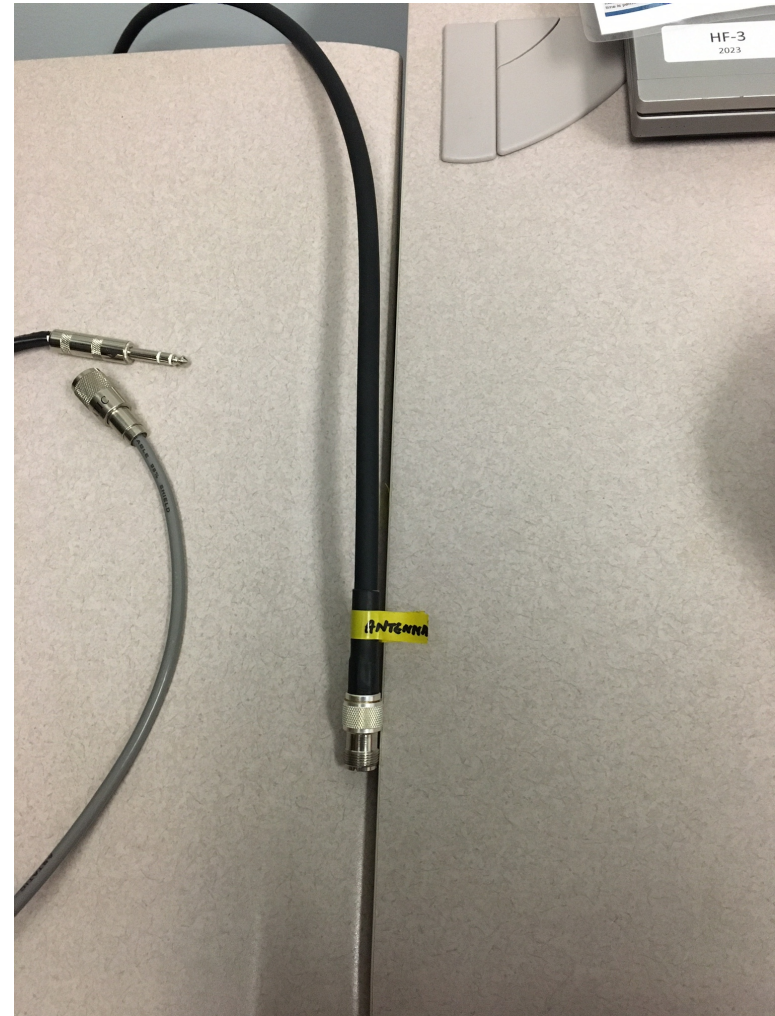- Exactly ONE HF coaxial cable with which to work....
- At Summer Field Day we had SEVEN Antennas & 7 coaxes....
- At the EOC for Winter Field Day....only 1






Then we heard about “Triplexers”

- Designed to allow 3 transmitters to use a single Yagi simultaneously

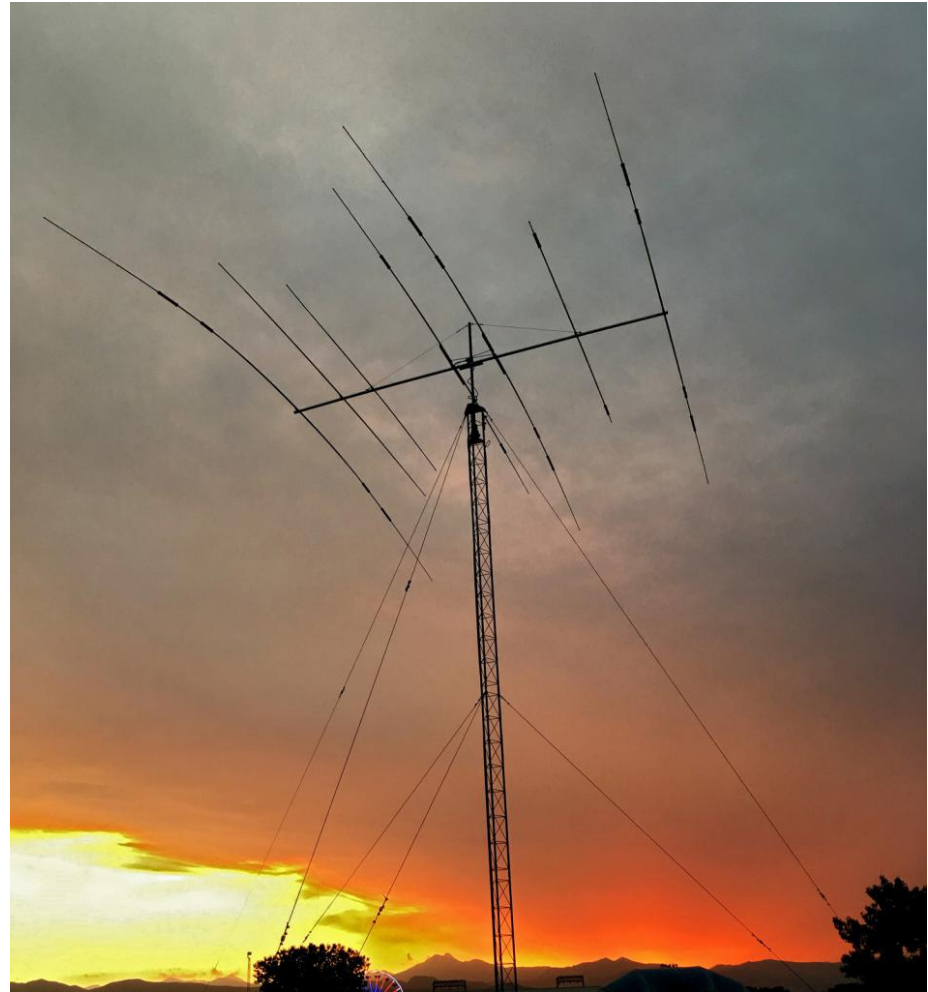REF: <https://www.mosley-electronics.com/>



Gary Gordon Starrted it all...2010



Jun 2010 QST - Copyright © 2023 American Radio Relay League, Inc. - All Rights Reserved

HF Yagi Triplexer Especially for ARRL Field Day

*This easy-to-build project lets up to
three transceivers on 10, 15, and
20 meters share the same antenna.*

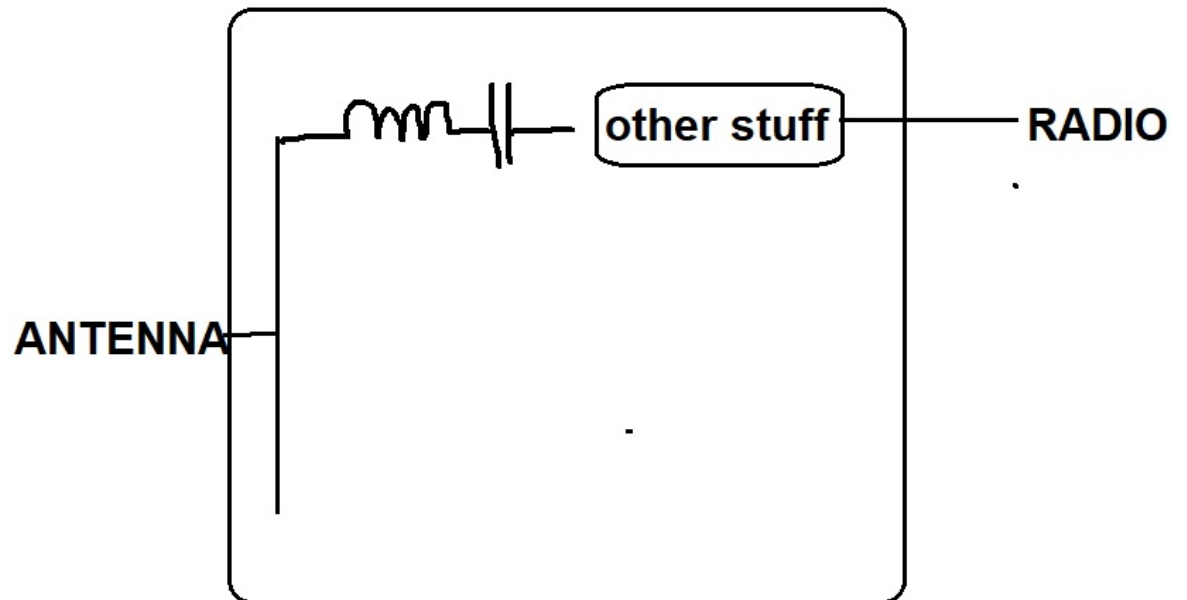
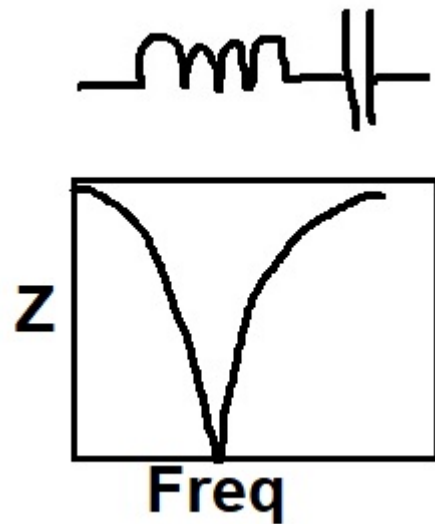
Gary Gordon, K6KV

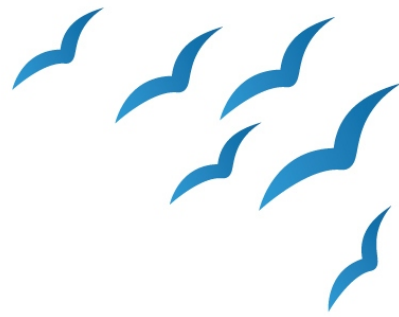


Figure 1 — Kenneth Finnegan, W6KWF, in foreground and Phil Verinsky, W6TQG, at Phil's station, competing in the July 2009 NAQP contest in the multioperator two transceiver category. Using the triplexer standing on the table between them, Kenneth and Phil operate on both 20 and 15 meters sharing Phil's triband antenna.




Series Tuned Filters Separate Sections






Original Simple Design

Series tuned separators

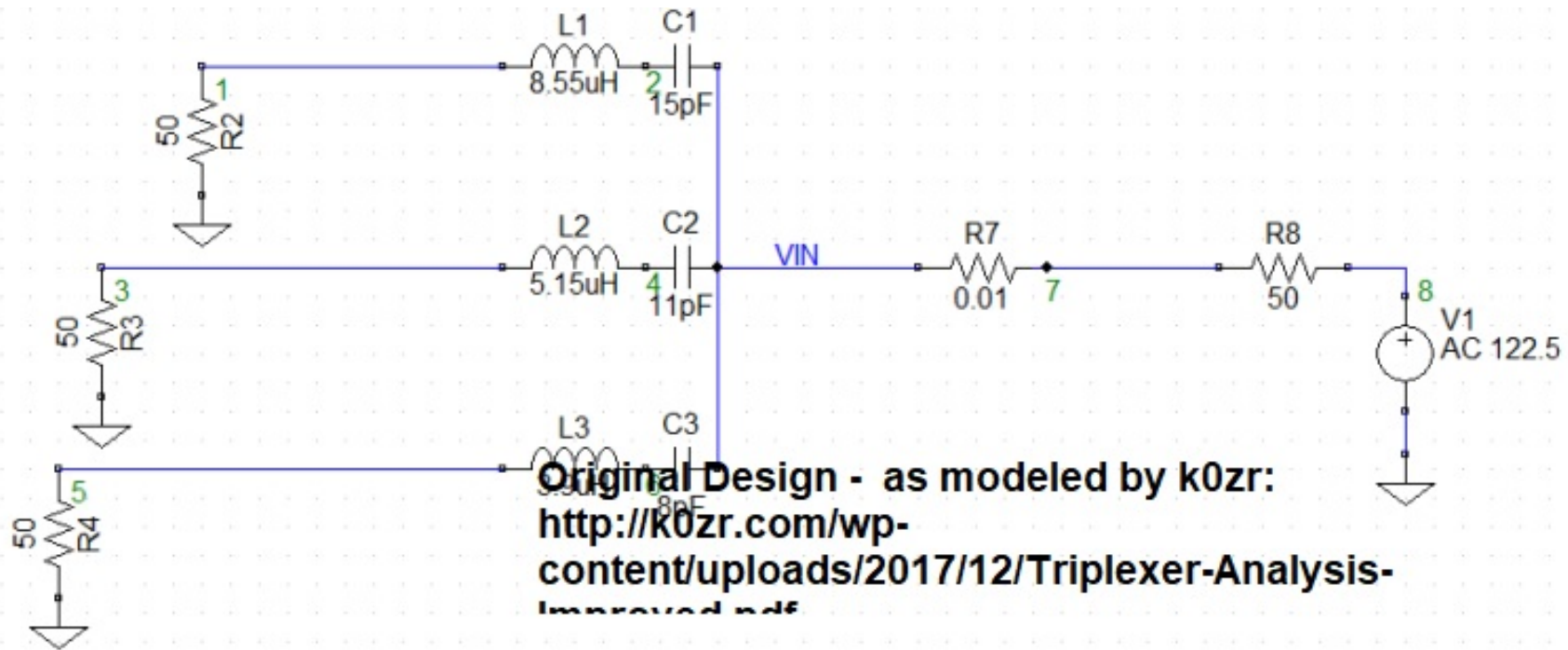

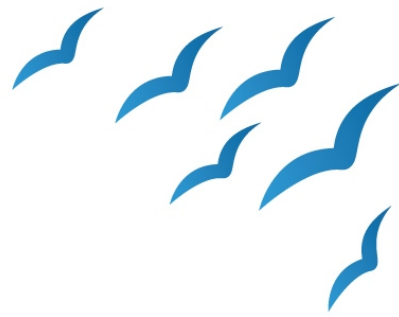

Requires: 2 sets of filters

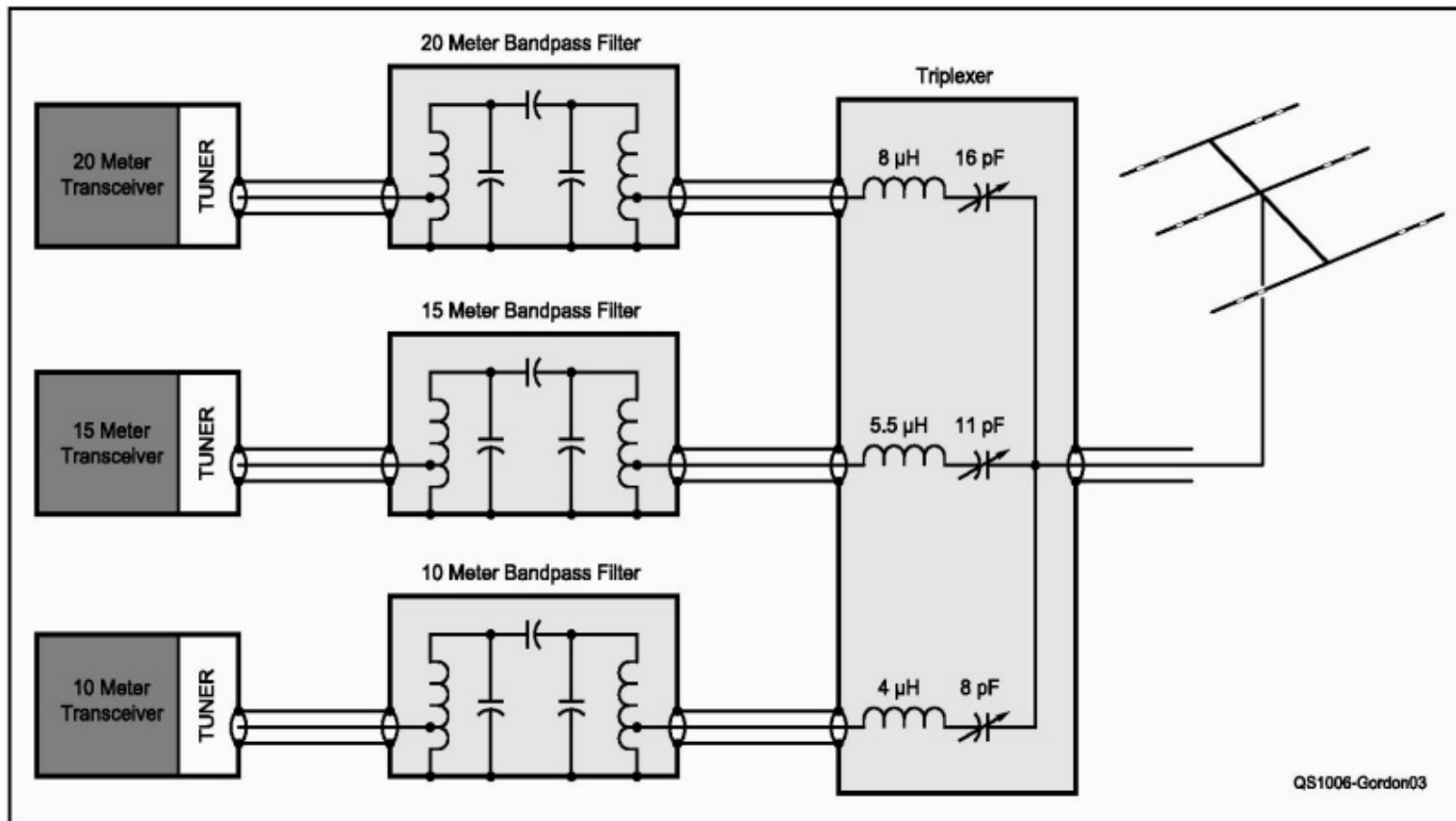


Figure 2 — Triplexer schematic. See the article regarding choosing the capacitors and winding the inductors.


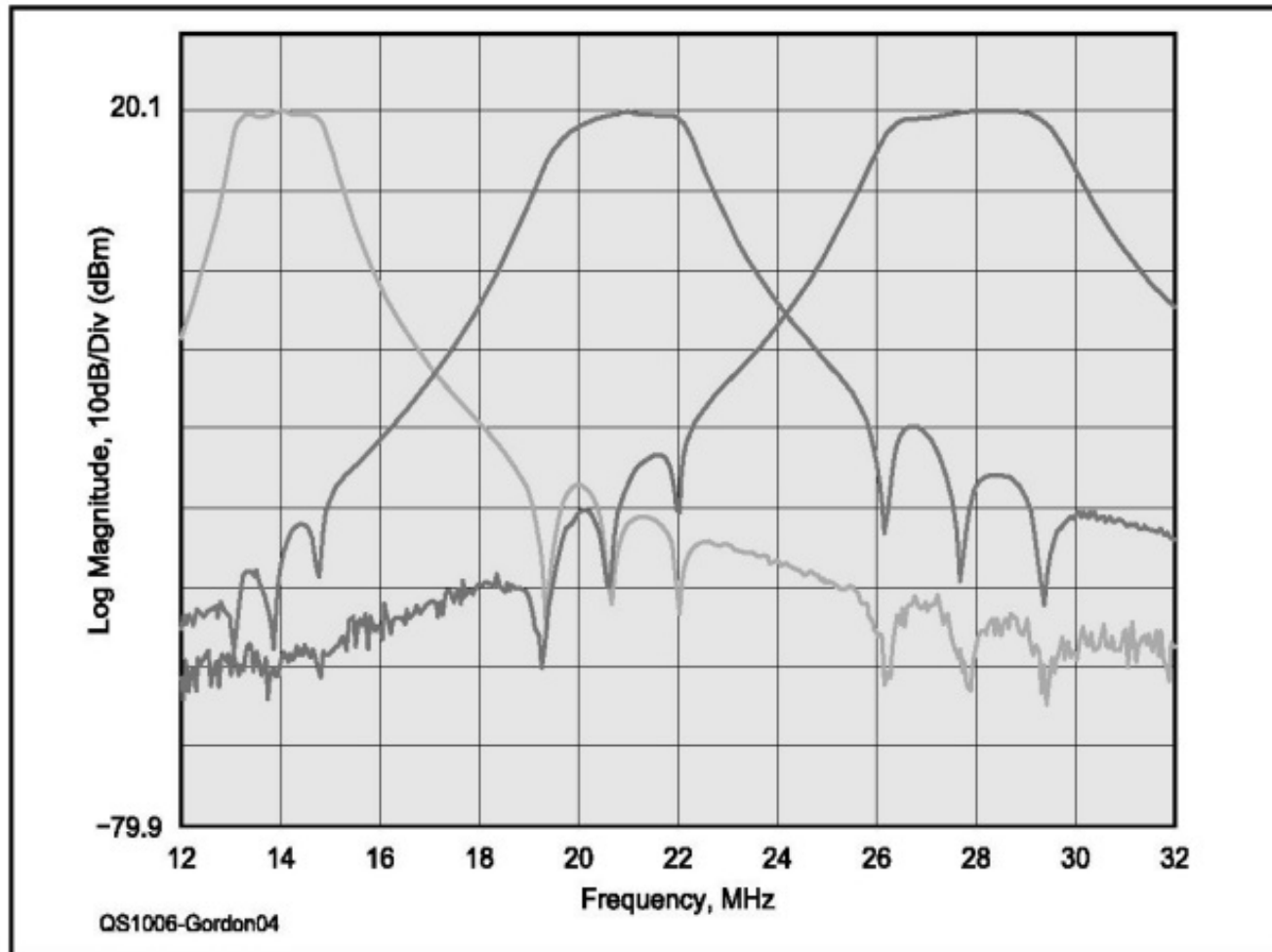


Figure 3. Frequency response of the triplexer decoupling network and band-pass filters. Next-band signals are attenuated by approximately 50 dB.


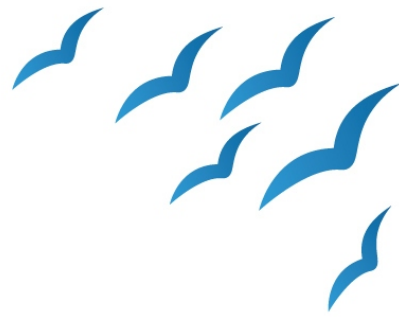
OVERALL RESPONSE INCLUDING BANDPASS FILTERS



Power Levels


- 100 Watts = +50 dBm
- 0.6V pk forward biases a diode, might cause damage.
 $P = (0.42V_{rms})^2 / 50 = 3.5 \text{ mW} = 5.5 \text{ dBm}$
- **DAMAGE Threshold = -45 dB separation**
- $S9+20 = 0.5\text{mV} = -73 \text{ dBm}$unlikely we can get -120dB separation....
- 60 dB separation yields -10 dBm = 100uwatt = 70 mV
→ not damaging, possibly tolerable on a separate band?

VA6AM Triplexer – KIT Available!

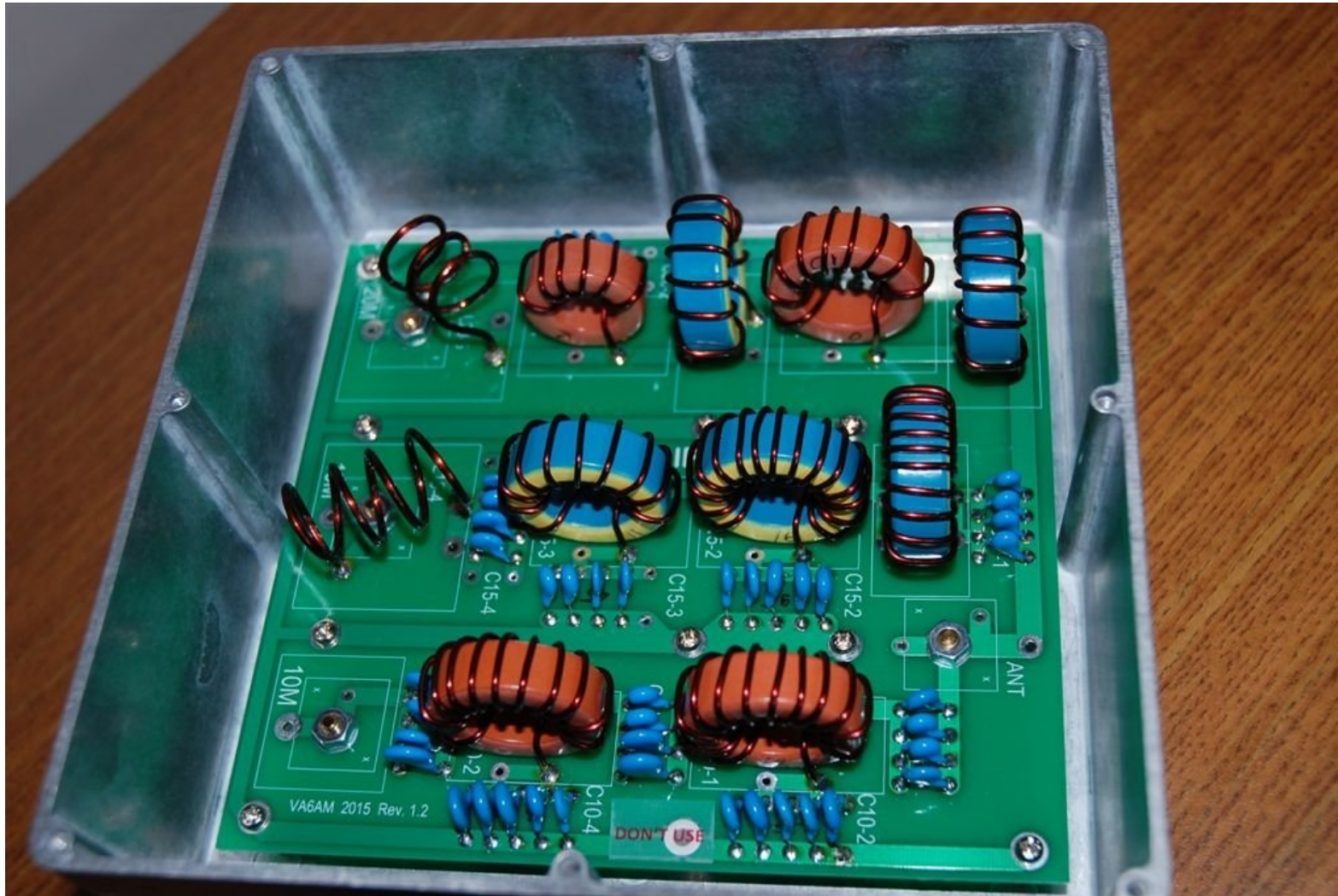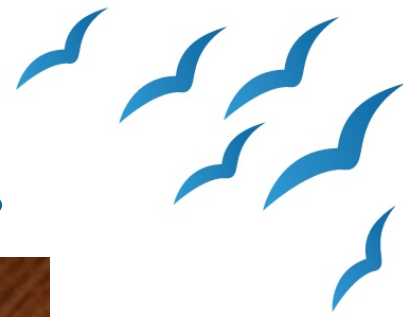



<https://va6am.com/2017/01/20/low-power-triplexer-assembly/>

Our First Efforts

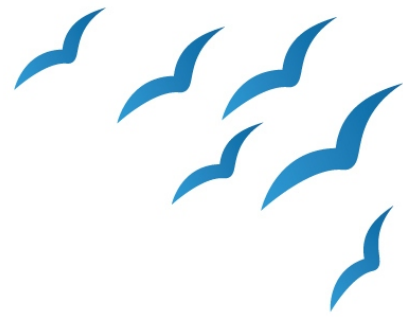


NanoVNA extremely helpful. Amazing how much you can do by pushing and pulling the Turns on a toroid! Introduced to BIG toroids and BIG wire – much lower losses.

Triplexer Building Schematic

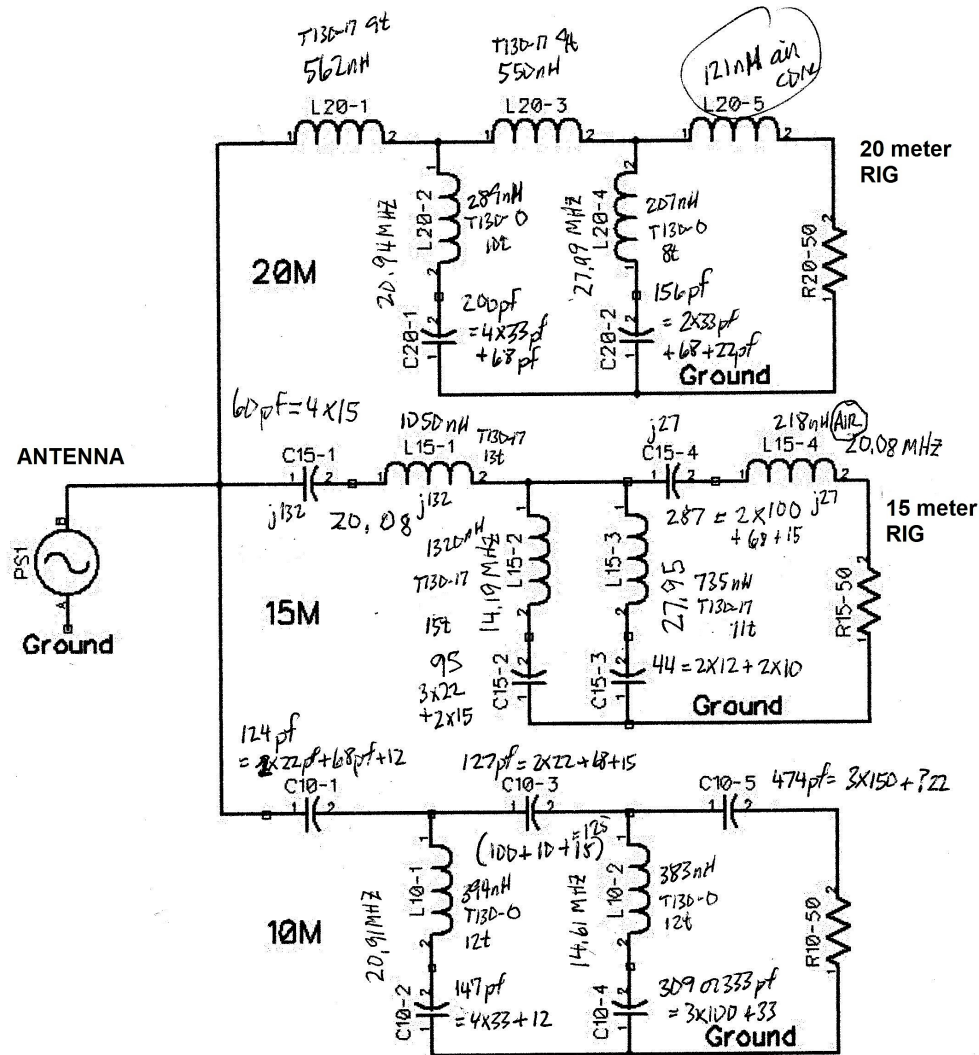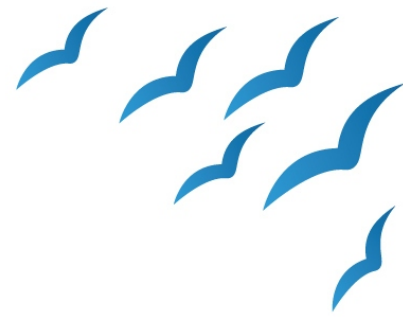


Caps, inductors marked

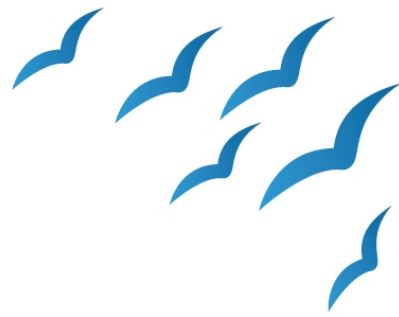


Original Build

	BAND		
Measurement (beginning)-> end values	20 meters	15 meters	10 meters
SWR into 50 ohms on antenna terminal	(1.067)-> 1.03	(1.33)-> 1.19	(1.26)-> 1.1
Passband loss	(0.49)-> 0.2 dB	(0.28)-> 0.18 dB	(0.49)-> 0.29dB
Isolation from lower interfereing frequency transmitter	(37)-> 38 dB	(37.5)-> 31 dB	(55)-> 42 dB

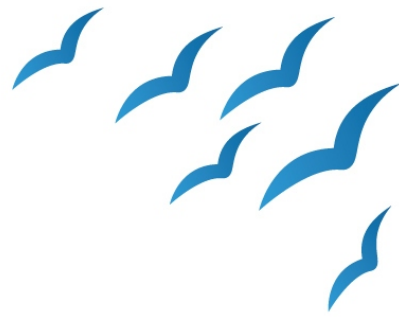

Need additional filtering!

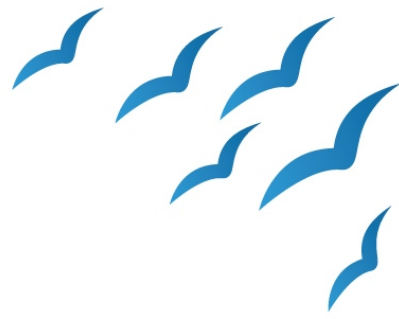- 38dB is way short of 60 dB requested
- Add 20+ additional BandPass Filtering (a stretch for our simple Butterworths)




Need to add another band

- 20/15/10 is not going to cut it as the sun lowers...
- Need 40 meters for certain,
- Want 80 meters also....



How Pavel's Traps Combine...

(15 meter filter example)


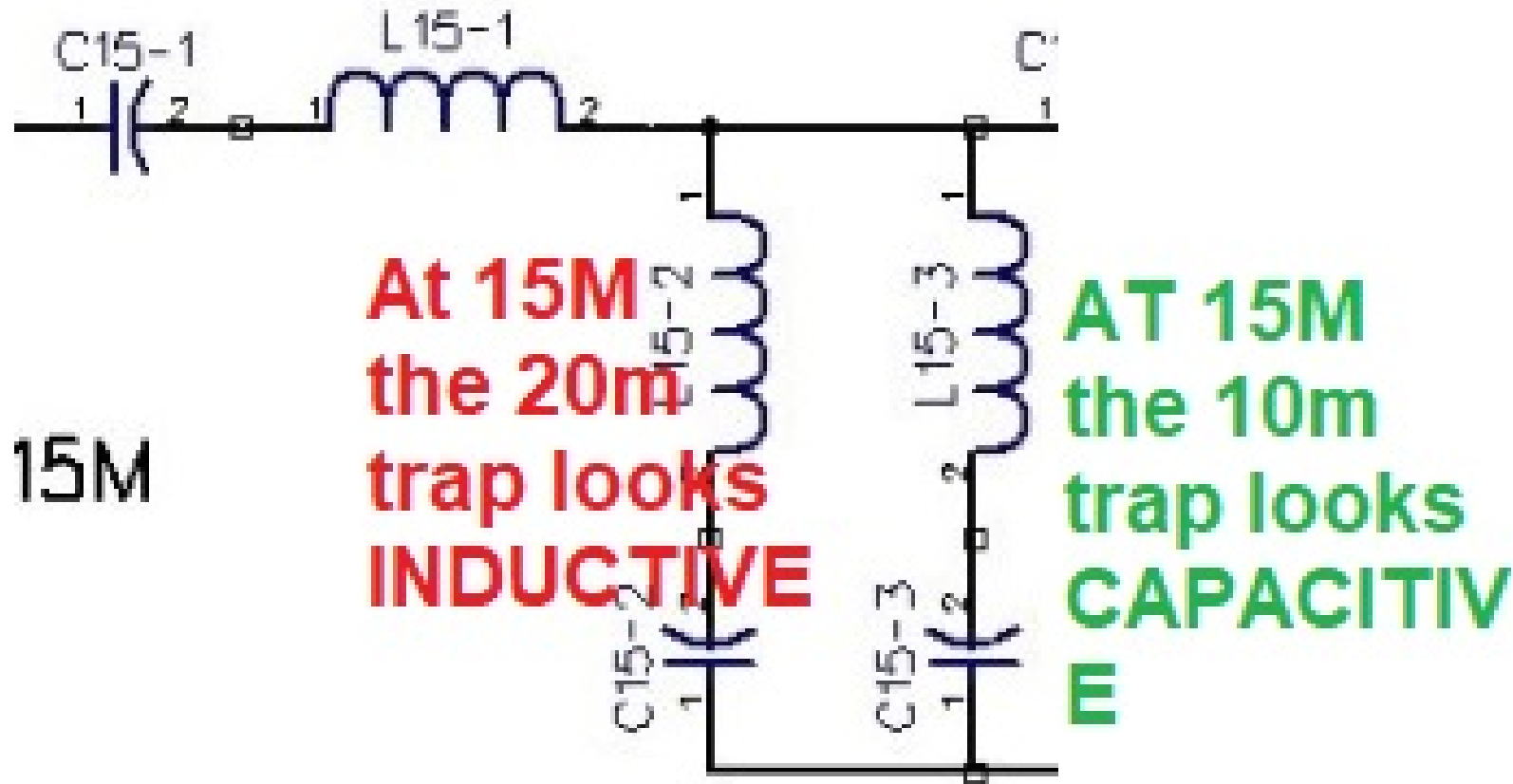




Must rework Pavel's 20m

- 10m = High Pass
- 15m = Bandpass (tricky combination of traps)
- 20m = Low Pass
- To achieve additional bands, 20m must become bandpass....


Making 20M bandpass work...

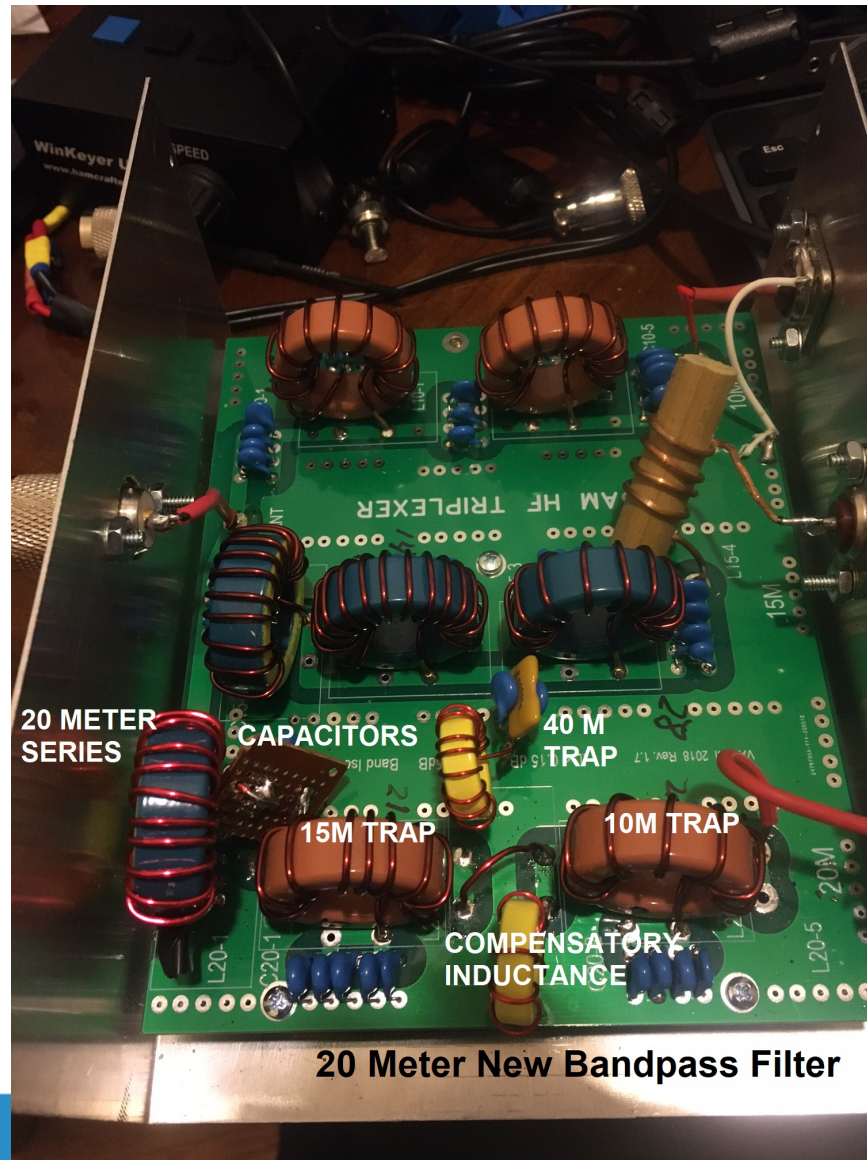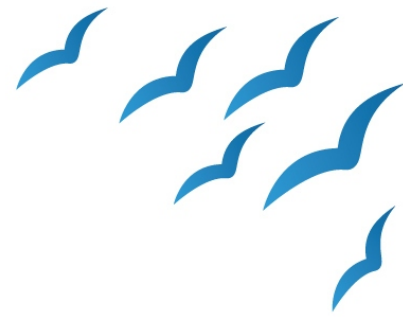

20 Meter New Bandpass Filter




Our 20M reworked filter

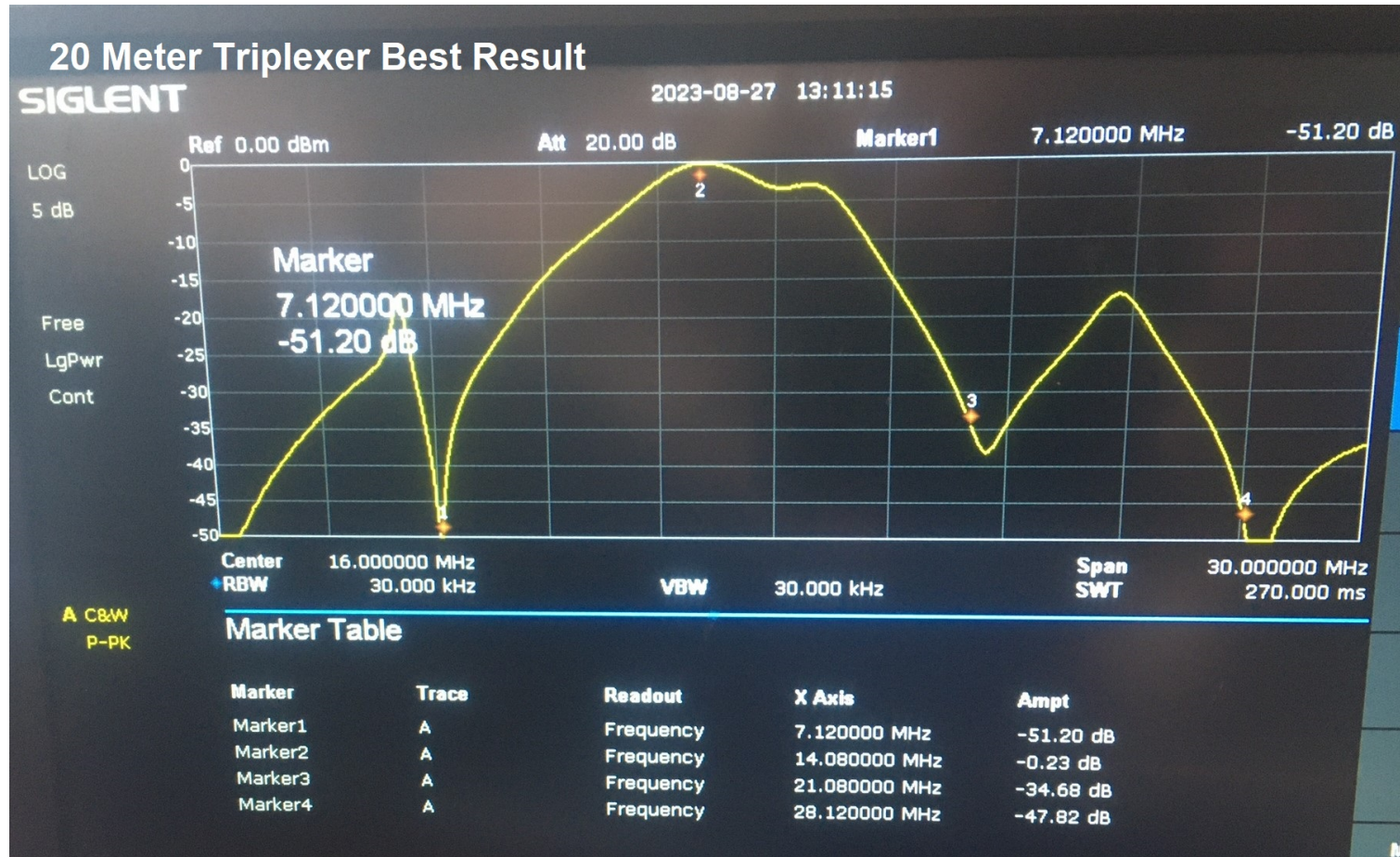





Showing PreCalc Students

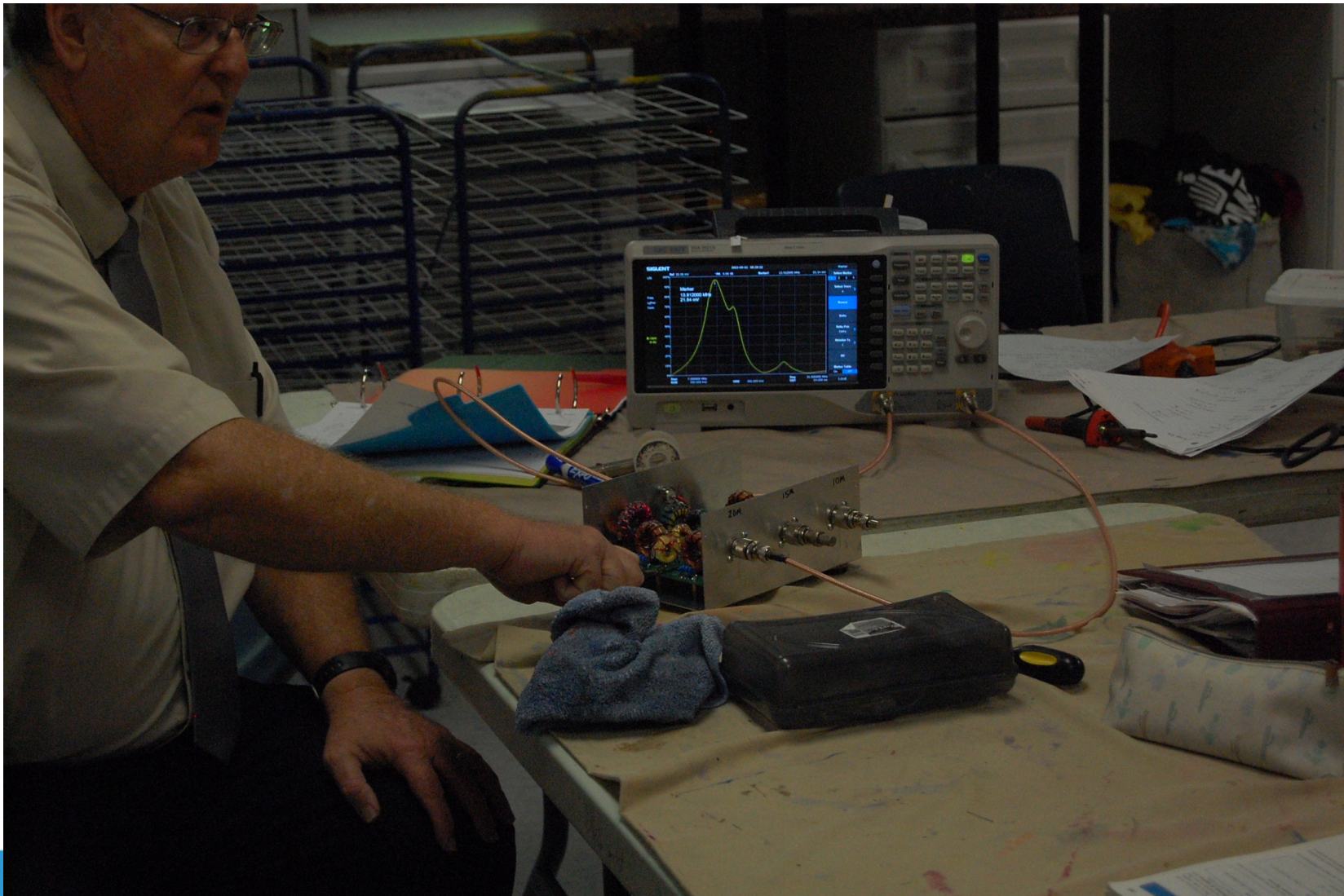

How Pavel Does Diplexer

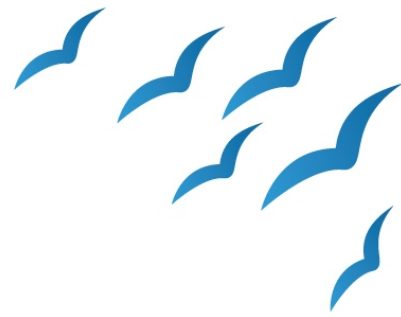


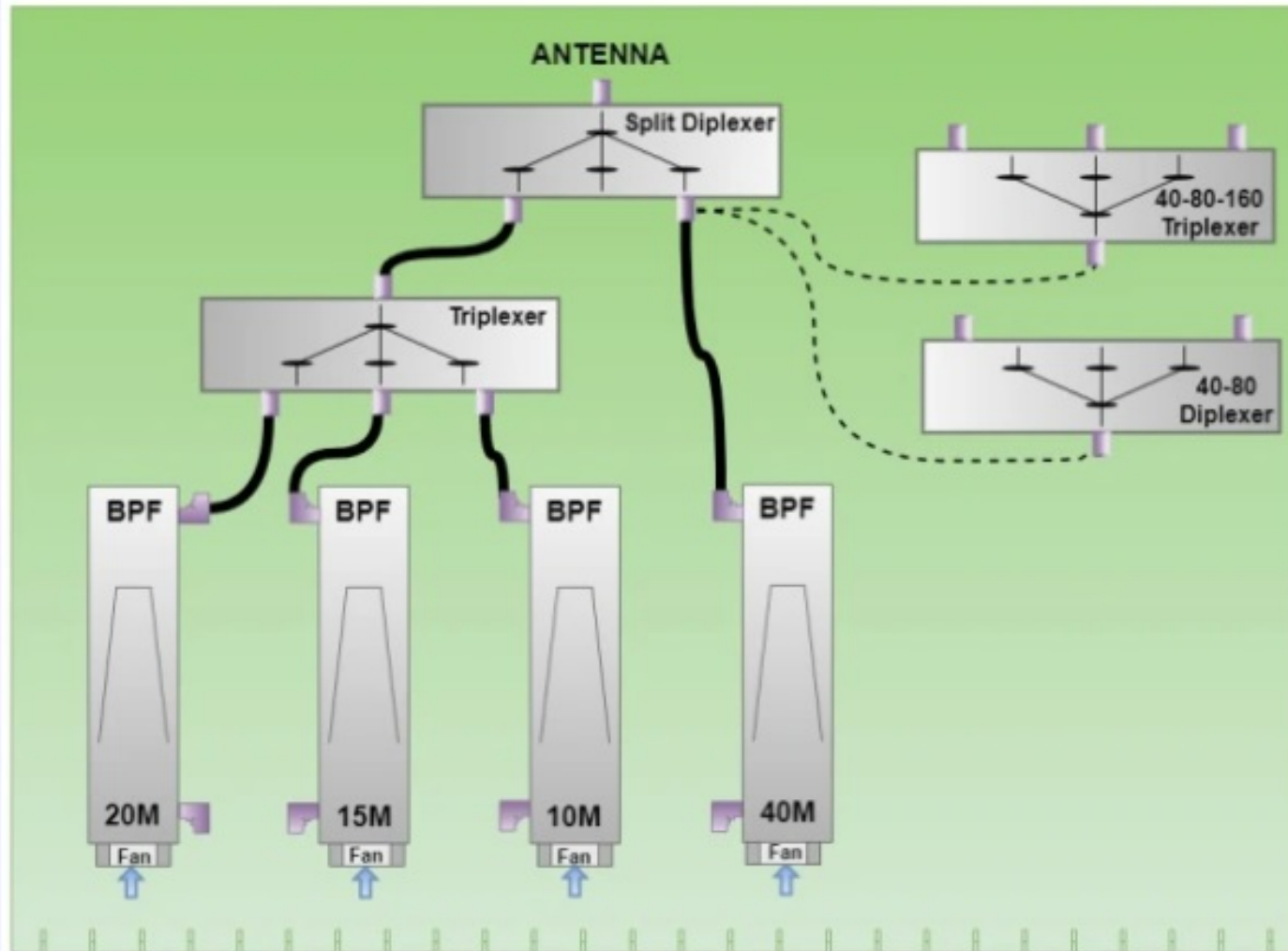Simple Diagram of Multi-Band Antenna Filter System




VERY
EXPENSIVE!!!

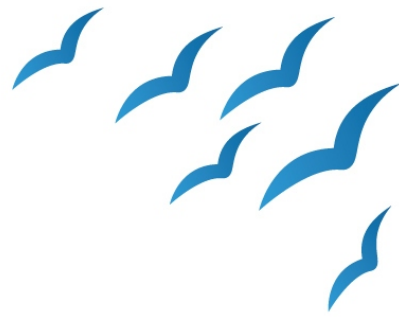We wanted merely to
expand the Triplexer
and avoid having to
add a diplexer in
front....



40M Triplexer Plan

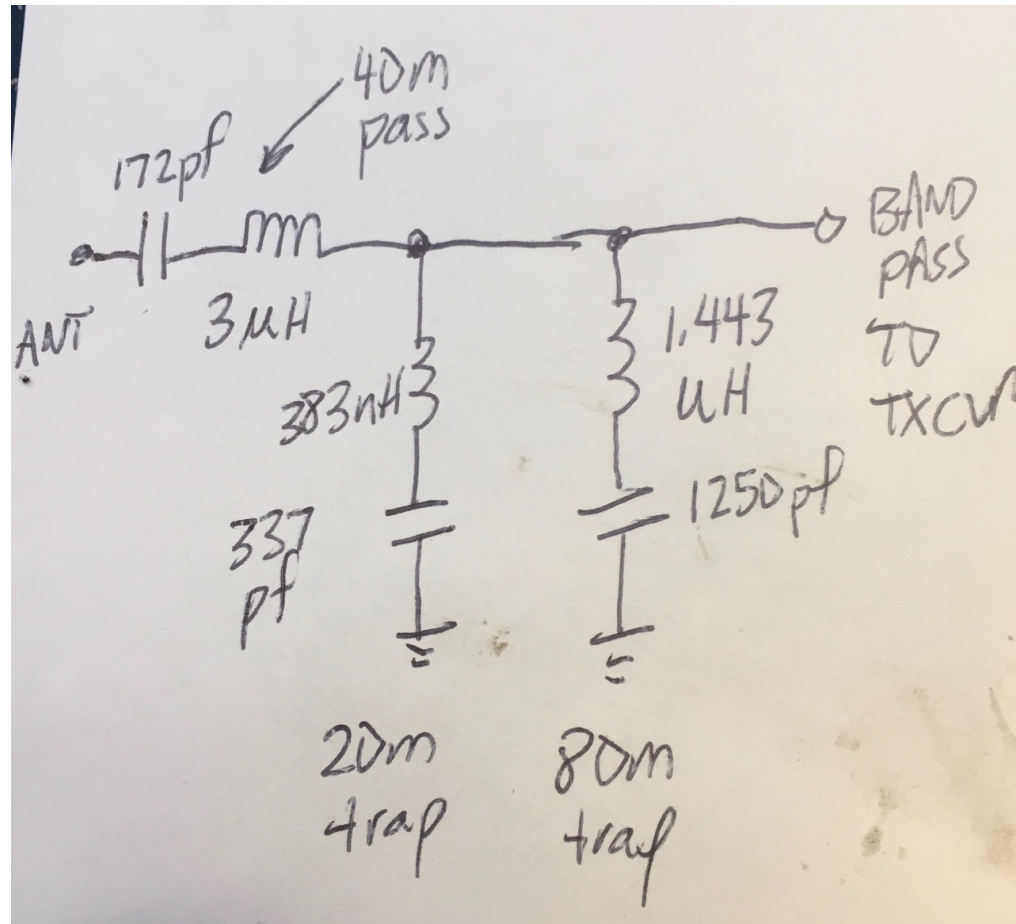




40 Meter BandPass Development

40-meter: must be a BANDPASS design. Pavel tends to put in 130-ish ohms of reactance at the passband frequency for each of his series reactances. 40-meter series tuned filter should be about 172 pf and $3\mu\text{H}$. For 100watts, it should be on a T130-17 toroid, #16 wire, approximately 27turns (46"). Two series traps to ground are chosen to approximately quash the 20meter energy and the 3.75 MHz energy, but combined to a parallel resonance on 40 meters.

40 Meter MultiPLEXOR	Series Tuned Input	20 meter trap	3.75 MHz trap
Inductor	$\sim 3\mu\text{H}^*$	383 nH*	1443 nH
ACTUAL TURNS in our instance	23 turns T130-17	8 turns T130-17	15 turns T130-17
Capacitor	$\sim 160\text{ pf } \geq 1\text{kV}$	$\sim 337\text{ pf } \geq 1\text{kV}$	$\sim 1250\text{ pf, } \geq 1\text{kV}$




Our 40 Meter Added Filter

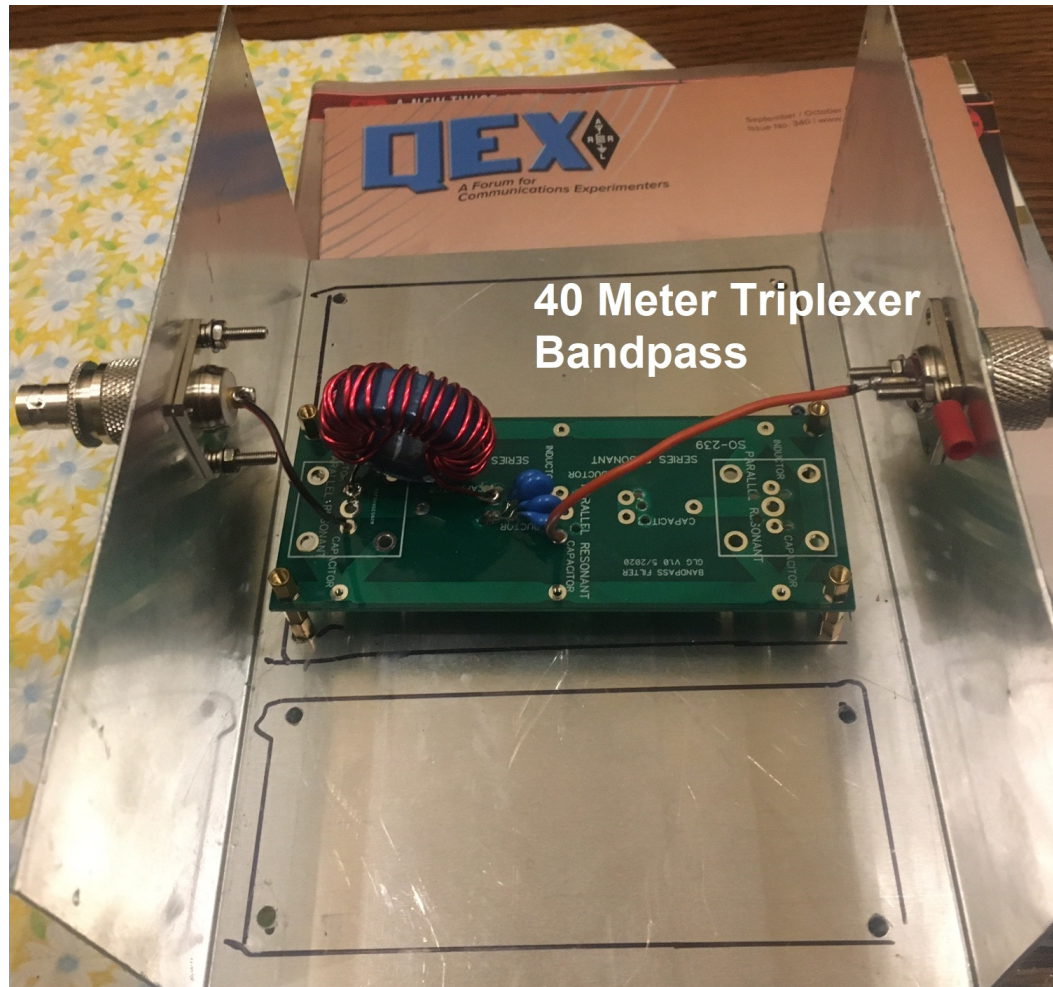




40 Meter Response



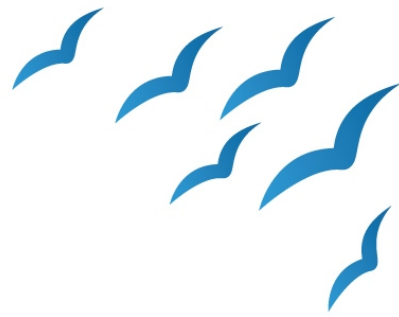


QuadPlexer Outcome

PASSBAND	40 meters	20 meters	15 meters	10 meters
Loss Measurements	Estimates of "additional required" are based on a minimum of 50dB separation required for possible reception and good safety.			
80 meters	~ -28 dB (need 22+ addnl dB)			
40 meters	0.36 dB	-51 dB (need 0+ dB addnl)	-21 dB (need 29+ dB addnl)	-29 dB (need 21+ addnl)
20 meters	-57 dB (adequate)	-0.23 dB	-32 dB (need 18 dB addnl)	-44 dB (need 6+ addnl)
15 meters	-24 dB (need 26 dB addnl)	-34 dB (need 16+ dB addnl)	-0.49 dB	-31 dB (need 19+ addnl)
10 meters	-24 dB (need 26 db addnl)	-48 dB (need 2+ dB addnl)	-37 dB (need 13 dB addnl)	-0.43 dB

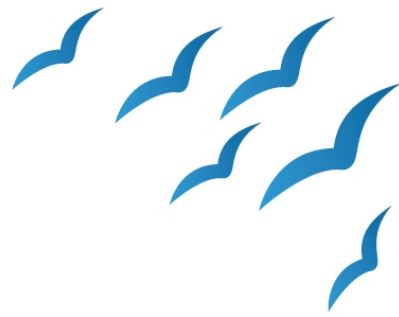


Add 80? 80/160 LPF - Pavel

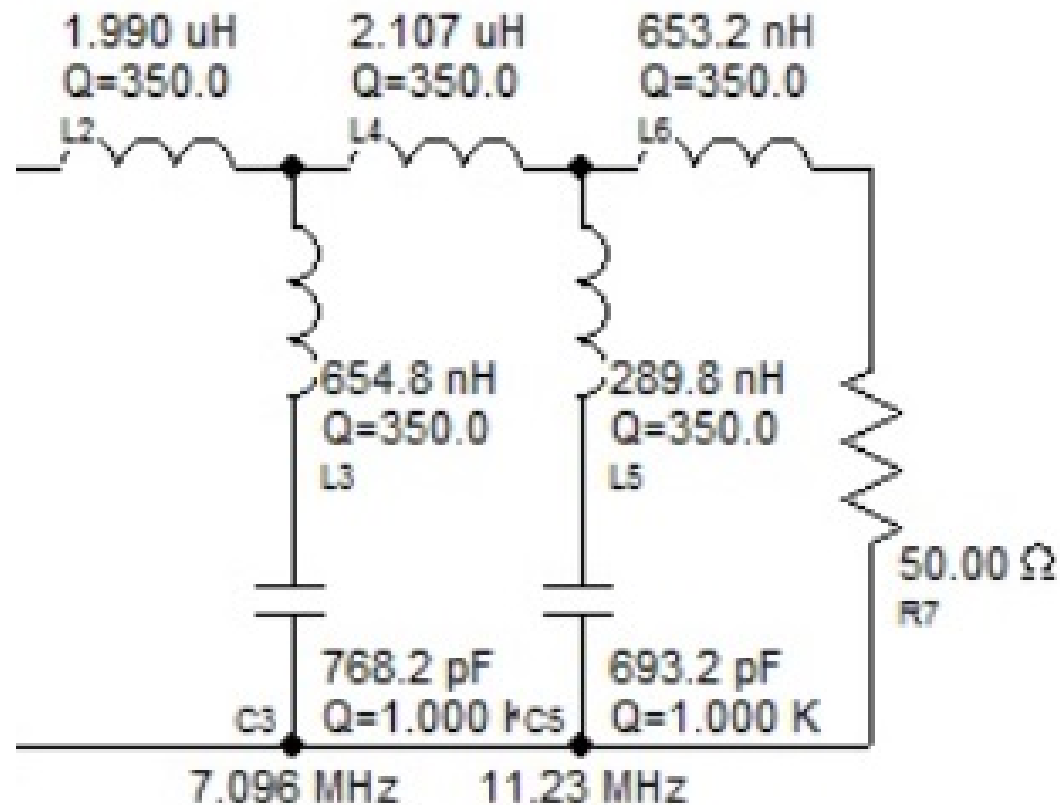

VA6AM LPF for 80 & below

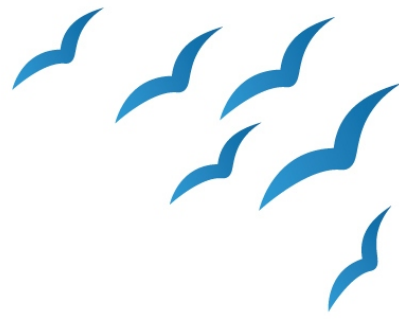see: <https://va6am.com/2017/01/01/4080-band-diplexer/>



Our wimpy 80/160 LPF result


LPF instead of BPF.

Built external LPF as well...not a bandpass...

Could not operate 160 at same time as 80...

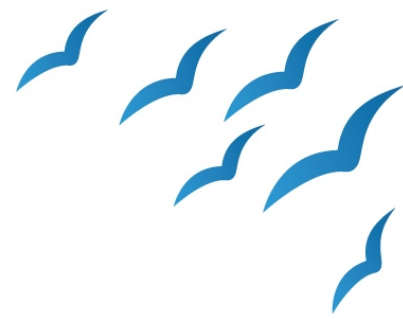
During WFD, 160 was taken over by an international CW contest...so didn't matter that much...






Two Boxes (connect w/coax)



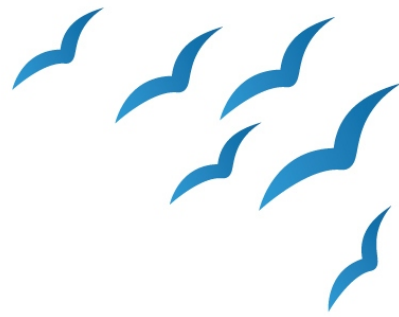

Bare QuintPlexor Response

Signal at common Antenna connector	80/160	40 meters	20 meters	15 meters	10 meters
Operating BAND PORT					
80/160m	-0.35 dB	-42 dB	-22 dB	-24 dB	
40 meters	-27 dB	~ -0.35dB	-47	est -20 dB	
20 meters		-57 dB	-0.23 dB	-32 dB	-44 dB
15 meters		-24 dB	-34 dB	-0.49 dB	-31 dB
10 meters		-24 dB	-48 dB	-37 dB	-0.43 dB

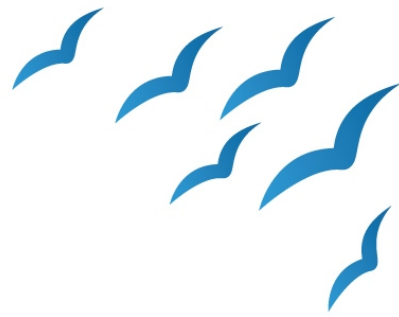


HV Capacitor Sourcing

Possible Sources of RF / HV Capacitors		
Capacitance	Rated Voltage	Link to potential source
100 pf and higher values	1kv	https://www.amazon.com/gp/product/B08BFWG5T7
220 pf silver mica	500V	https://www.amazon.com/gp/product/B00L5YM4X6
Assorted	supposedly 500V	https://www.amazon.com/gp/product/B01INRL2WQ Be careful -- not all of these are 500v
TDK 47pf	6kV	https://www.digikey.com/en/products/detail/tdk-corporation/CC45SL3JD470JYVNA/7383672
TDK 22pf	6kV	https://www.digikey.com/en/products/detail/tdk-corporation/CC45SL3JD220JYGNA/7383661
TDK 10pf	6kV	https://www.digikey.com/en/products/detail/tdk-corporation/CC45SL3JD100JYNNA/4457596



“Filter Room”



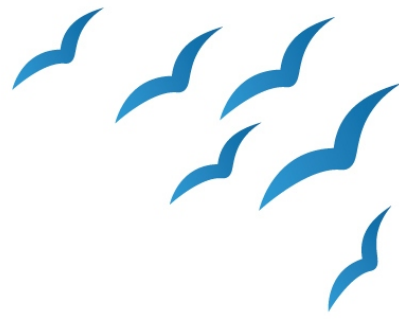


300W visible!







Pounding on Filters with 3x100W




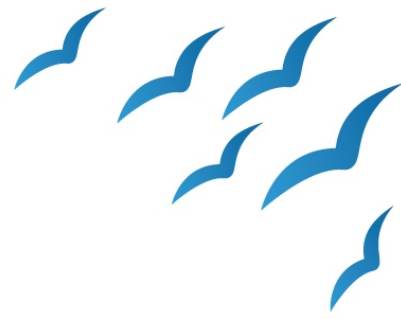


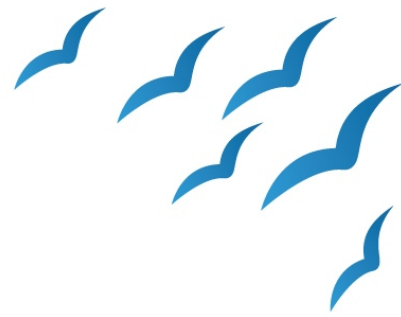

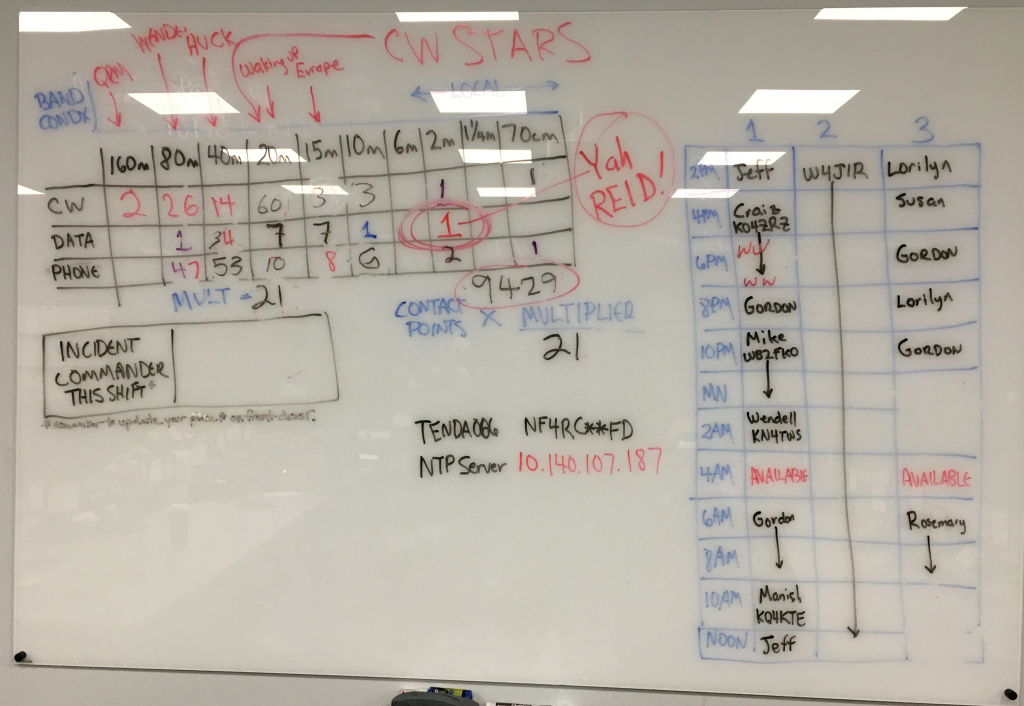

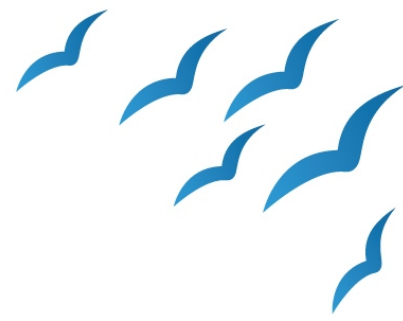First ever CW contact...
can't copy CW....
why let that stop you?



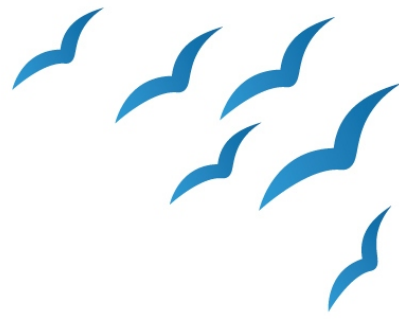


OOPS! “I smell SMOKE!”


Manish Sahni KQ4KTE

15 meter bandpass filter had long been “suspect”....rapidly changing SWR....


2/3 of the way into winter field day....it gave up the ghost.

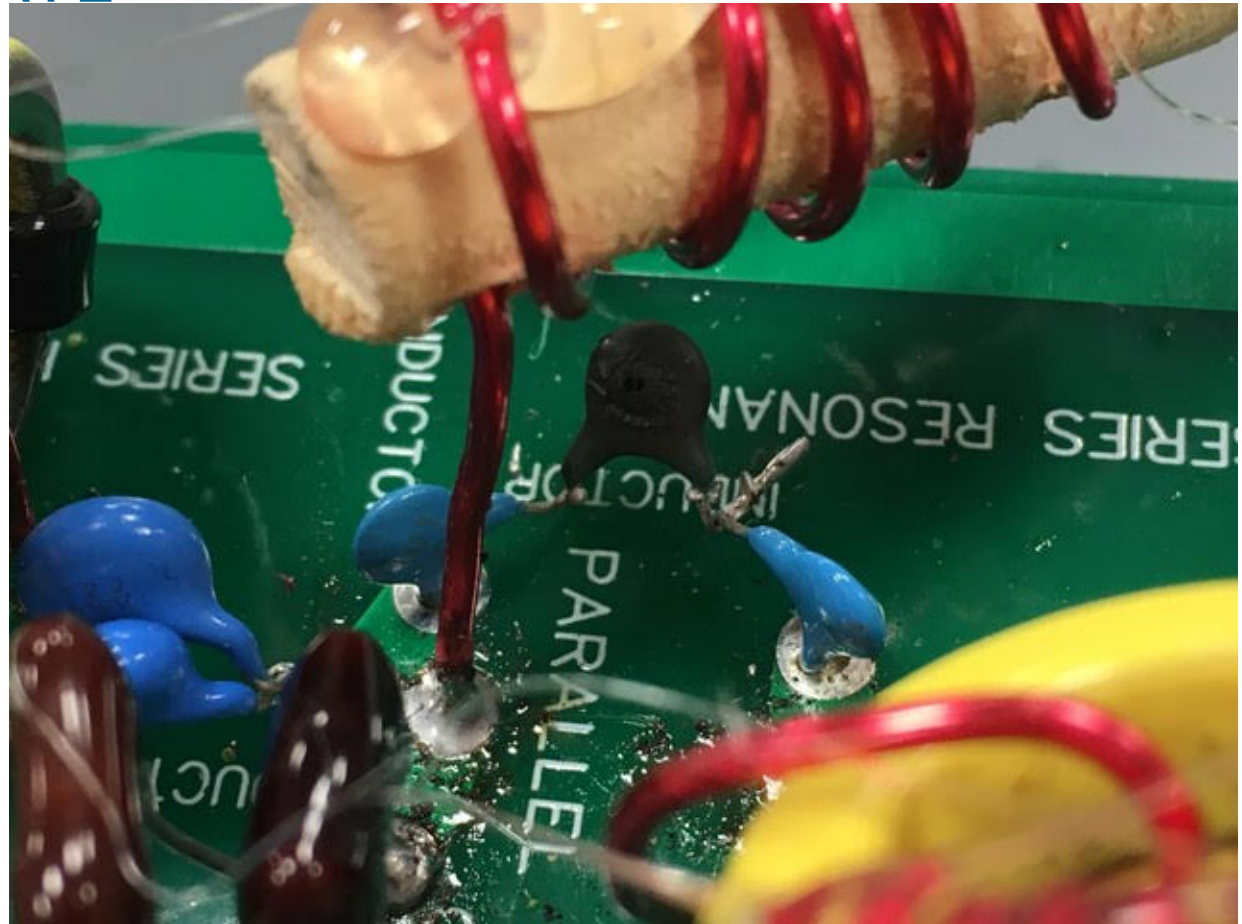Believe it or not, we had it repaired and back on the air with better outcome in about 30 min




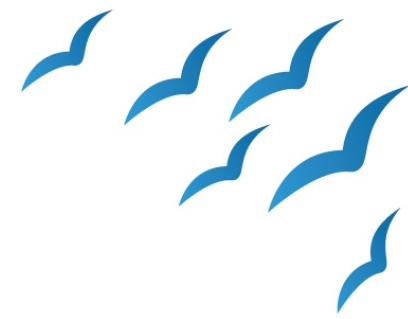


Total CW Contacts	111
Total Phone Contacts	129
Total DIG Contacts	64
Total Multiplier	21
Total Score	10,059
Total on-site operators	13
Primary off-site contacts	1 (K9RFT)

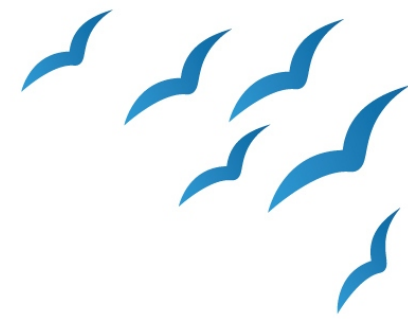

CONTACTS EACH HOUR BY METHOD

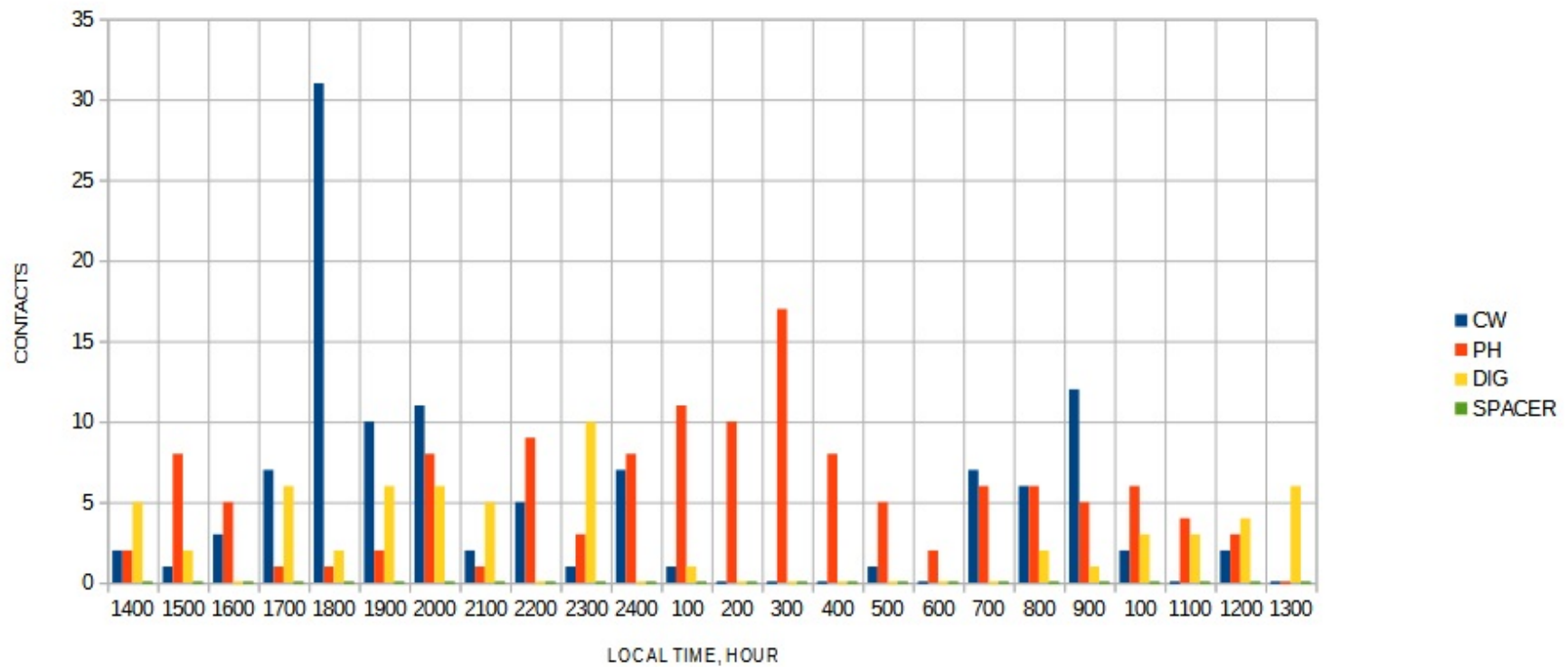

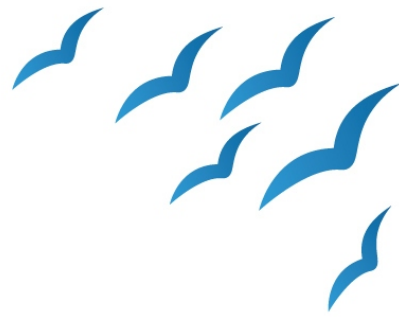

Conclusions

- Replace the 15m bandpass with a Pavel Kit
- T130 sized toroids much better than T80!
- Bigger wire much better than #18!
- 3kv/6kv caps much better than mica 500V
- You really want 60dB separation
- We want a YAGI!
- Add separate 160m tap?